

# Integrated System Architecture

## Lab session 3 report - RISC-V special project

Marco Andorno (247222)  
Michele Caon (253027)  
Alessio Colucci (251197)  
Matteo Perotti (251453)

March 20, 2019

## Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
1.1	Pipeline structure . . . . .	3
<b>2</b>	<b>Datapath</b>	<b>3</b>
2.1	Register file . . . . .	3
2.2	ALU . . . . .	4
2.2.1	ALU decoder . . . . .	6
2.3	Branch and Jump management . . . . .	6
2.3.1	Types of instructions . . . . .	6
2.3.2	Instruction execution . . . . .	8
2.3.3	Effective calculation . . . . .	8
2.3.4	Next address selection CU . . . . .	9
2.3.5	Next address generation . . . . .	9
<b>3</b>	<b>Control</b>	<b>10</b>
3.1	Forwarding Unit (FWU) . . . . .	10
3.1.1	Load/store forwarding . . . . .	10
3.2	Hazard Detection Unit (HDU) . . . . .	11
3.2.1	Inserting a NOP . . . . .	12
3.3	Control Unit (CU) . . . . .	12
3.4	Immediate Generator (ImmGen) . . . . .	12
<b>4</b>	<b>Main architecture</b>	<b>15</b>
<b>5</b>	<b>Simulation</b>	<b>15</b>
5.1	Memory . . . . .	15
5.2	Testing procedure . . . . .	15
5.2.1	Testbench . . . . .	17
5.2.2	Single instructions test . . . . .	17
5.2.3	Branches and control hazard test . . . . .	18
5.2.4	Data hazards and forwarding . . . . .	19
5.2.5	Complete program test . . . . .	19
5.3	Assembler . . . . .	23

## 1 Introduction

The aim of this laboratory session is to design a simple RISC-V core implementing the RV32I instruction set in SystemVerilog, which is the basic 32-bit integer-only set of instructions, without multiply and divide. The complete set is shown in figure 1.

imm[31:12]					rd	0110111	LUI
imm[31:12]					rd	0010111	AUIPC
imm[20:10:1 11 19:12]					rd	1101111	JAL
imm[11:0]			rs1	000	rd	1100111	JALR
imm[12:10:5]		rs2	rs1	000	imm[4:1 11]	1100011	BEQ
imm[12:10:5]		rs2	rs1	001	imm[4:1 11]	1100011	BNE
imm[12:10:5]		rs2	rs1	100	imm[4:1 11]	1100011	BLT
imm[12:10:5]		rs2	rs1	101	imm[4:1 11]	1100011	BGE
imm[12:10:5]		rs2	rs1	110	imm[4:1 11]	1100011	BLTU
imm[12:10:5]		rs2	rs1	111	imm[4:1 11]	1100011	BGEU
imm[11:0]			rs1	000	rd	0000011	LB
imm[11:0]			rs1	001	rd	0000011	LH
imm[11:0]			rs1	010	rd	0000011	LW
imm[11:0]			rs1	100	rd	0000011	LBU
imm[11:0]			rs1	101	rd	0000011	LHU
imm[11:5]		rs2	rs1	000	imm[4:0]	0100011	SB
imm[11:5]		rs2	rs1	001	imm[4:0]	0100011	SH
imm[11:5]		rs2	rs1	010	imm[4:0]	0100011	SW
imm[11:0]			rs1	000	rd	0010011	ADDI
imm[11:0]			rs1	010	rd	0010011	SLTI
imm[11:0]			rs1	011	rd	0010011	SLTIU
imm[11:0]			rs1	100	rd	0010011	XORI
imm[11:0]			rs1	110	rd	0010011	ORI
imm[11:0]			rs1	111	rd	0010011	ANDI
0000000		shamt	rs1	001	rd	0010011	SLLI
0000000		shamt	rs1	101	rd	0010011	SRLI
0100000		shamt	rs1	101	rd	0010011	SRAI
0000000		rs2	rs1	000	rd	0110011	ADD
0100000		rs2	rs1	000	rd	0110011	SUB
0000000		rs2	rs1	001	rd	0110011	SLL
0000000		rs2	rs1	010	rd	0110011	SLT
0000000		rs2	rs1	011	rd	0110011	SLTU
0000000		rs2	rs1	100	rd	0110011	XOR
0000000		rs2	rs1	101	rd	0110011	SRL
0100000		rs2	rs1	101	rd	0110011	SRA
0000000		rs2	rs1	110	rd	0110011	OR
0000000		rs2	rs1	111	rd	0110011	AND
0000	pred	succ	00000	000	00000	0001111	FENCE
0000	0000	0000	00000	001	00000	0001111	FENCE.I
000000000000			00000	000	00000	1110011	ECALL
000000000001			00000	000	00000	1110011	EBREAK
csr			rs1	001	rd	1110011	CSRRW
csr			rs1	010	rd	1110011	CSRRS
csr			rs1	011	rd	1110011	CSRRC
csr			zimm	101	rd	1110011	CSRRWI
csr			zimm	110	rd	1110011	CSRRSI
csr			zimm	111	rd	1110011	CSRRCI

Figure 1: RV32I instructions

Actually, not all the instructions were implemented as the support for an operating system and exception handling is beyond the scope of this experience.

The different formats of the instructions are shown in figure 2, which is useful reference in the rest of this report.

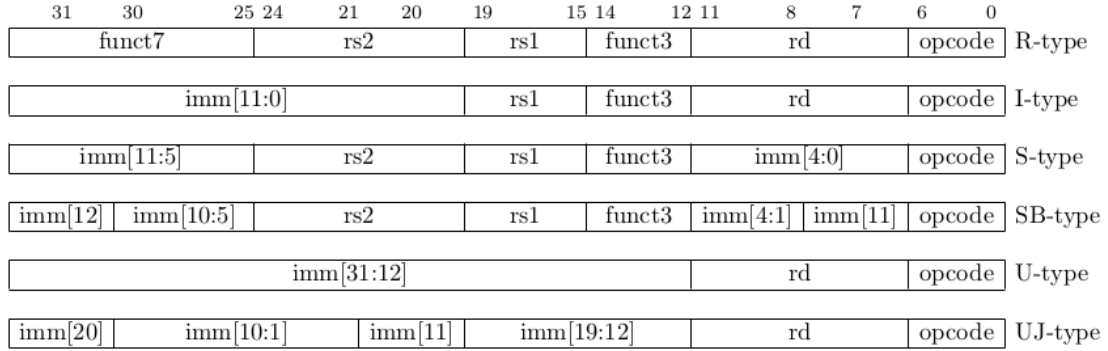


Figure 2.3: RISC-V base instruction formats showing immediate variants.

Figure 2: Instruction formats

## 1.1 Pipeline structure

From an architectural point of view, the design is based on the classic RISC 5-stage pipeline, divided as follows:

1. Instruction fetch (IF): the new instruction is read from the instruction memory, pointed by the current Program Counter (PC).
2. Instruction decode (ID): operands are read from the register file (RF), the control unit generates control signals for the following stages, immediate fields are extended on 32 bits and the ALU controls are decoded.
3. Execute (EX): the ALU performs the required operation and the new PC is computed in case of branch or jump.
4. Memory access (DMEM): the data memory is read or written for instructions that require so (load and stores), otherwise data just bypasses this stage.
5. Write back (WB): either the ALU result or the data memory output is written to the destination register, when required.

Pipeline registers separating each stage take the name of the two stages they are in between (e.g. ID/EX). Actually, assuming a synchronous memory interface, two of these registers are in part bypassed by the memory timing, in order to keep the number of stages at five. For more details on this matter, refer to section 5.1.

The following sections describe the different datapath and control blocks and the testing methodology.

## 2 Datapath

### 2.1 Register file

The RISC-V register file is composed of 32 registers, each 32-bit wide (for RV32I), called x0 to x31, where x0 is a special register hardwired to the value 0, which can turn useful for some instructions. Figure 3 shows the top level diagram of the register file structure.

Writes to the register file are, of course, synchronous and happen on the positive edge of the clock. For a correct write operation, the destination register must be selected using the `writeAddr`

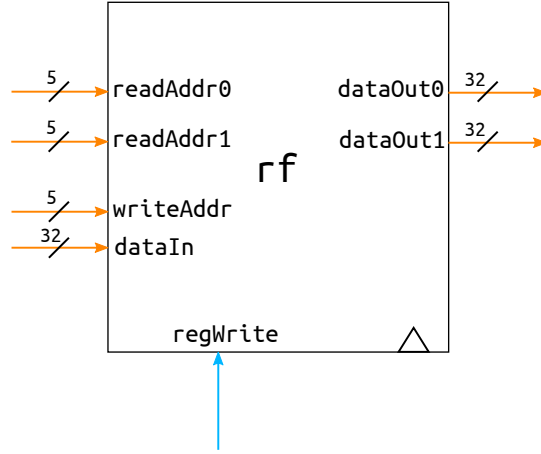


Figure 3: Register file

port, the input data must be placed on the **dataIn** port and the signal **regWrite** must be asserted. Internally, the register file will enable only the selected register using a decoder.

Reads are instead combinational and can occur on two different registers at a time, thanks to two different read ports. To select the correct output value, a 32-to-1 multiplexer is used on each read port. However, in order to avoid data hazards during the write back stage, the register file also implements bypassing of input data directly to the output if the same register is read and written during the same clock cycle. Figure 4 shows this read selection process (no multiplexer is used to select 0 in case the register being read is x0 as we can suppose it is hardwired directly at its output).

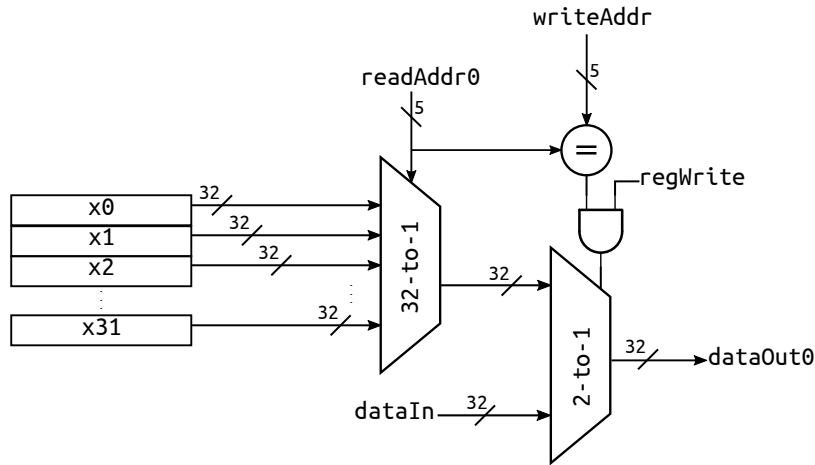


Figure 4: Read operation in the register file

To better illustrate the behavior of the register file operations, their timing diagram is shown in 5.

## 2.2 ALU

The ALU is in charge of performing all operations required by arithmetic and logic instructions, load and store, and branch comparison. Figure 6 shows its top level block diagram, which is simply composed of two inputs and one output on 32 bits, along with a 4-bit control signal to select the desired operation.

The complete list of operation that the ALU can perform is the following (in the order in which they are defined on the **ctl** input):

1. Add

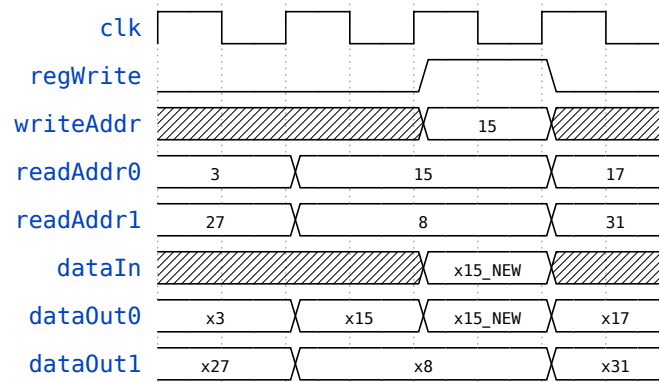


Figure 5: Register file timing

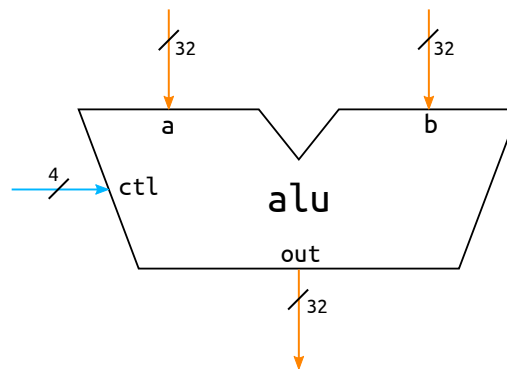


Figure 6: ALU

2. Subtract
3. AND
4. OR
5. XOR
6. Left shift
7. Right shift
8. Right shift with sign extension
9. Set if equal
10. Set if not equal
11. Set if less than
12. Set if greater or equal than
13. Set if less than unsigned
14. Set if greater or equal than unsigned
15. AUIPC (add current PC and left-shifted immediate)

Note that all operations were described behaviorally as per specifications, in order to be as implementation independent as possible and open to every optimization that a synthesis tool can perform.

All ‘set if \*’ operations set the output to the value 1 (0x00000001) if the condition is true, or 0 otherwise. This approach was chosen instead of using flags (such as Carry, Overflow, Negative and so on) to compute conditions as it was deemed simpler to implement and thorough enough, given that there would not have been other uses for the flags.

### 2.2.1 ALU decoder

The control input of the ALU is generated by a special decoder starting from the opcode, funct3 and funct7 fields of each instruction which requires an ALU operation, as described in figure 7. This block consists only of a series of conditional statements (that can easily be mapped to multiplexers) which select the correct control signal.

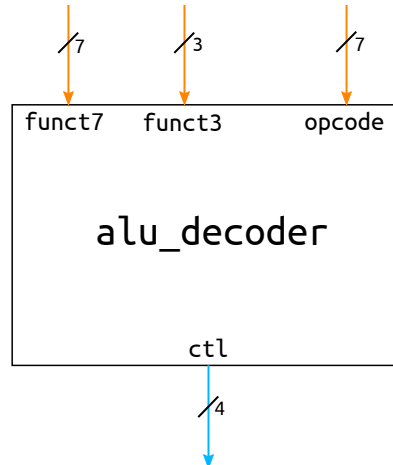


Figure 7: ALU decoder

Another approach would have been to split the control of the ALU into two decoding steps<sup>1</sup>, but a preliminary analysis concluded that no practical advantage would be obtained this way. Moreover, only few bits of the input fields are required to make a definite decision on the control output, but in order to keep modularity and continuity in the design, the whole fields are given in the interface of the block.

## 2.3 Branch and Jump management

A general view of the unit is given in figure 8, along with the significant datapath blocks involved.

### 2.3.1 Types of instructions

There are two classes of instructions which can lead to a modification of the sequential flow of the program. In the RV32I ISA they are:

1. Branches
2. Jumps

The former is a conditional change of the usual choice of the next address to be put in the PC, whereas the latter is unconditional. The condition, whenever present, is always based on the result of an ALU comparison.

**Branch** instructions exist in different flavours, depending on which comparison has to be performed between the content of two registers. Here follows a list of all of them:

1. BEQ (branch if equal)
2. BNE (branch if not equal)
3. BLT (branch if less than)
4. BGE (branch if greater or equal than)
5. BLTU (branch if less than unsigned)

<sup>1</sup>As suggested in Chapter 4 of D. Patterson, J. Hennessy, *Computer Organization and Design RISC-V Edition*, Morgan Kaufmann, 2017

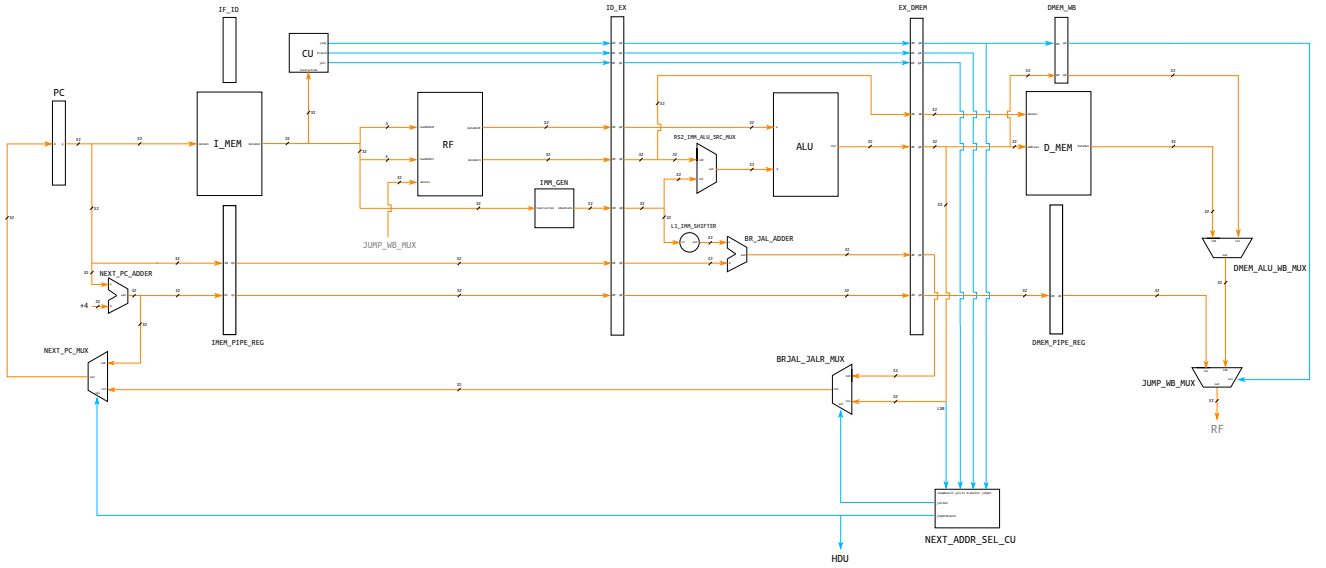


Figure 8: Branch and Jump management HW

## 6. BGEU (branch if greater or equal unsigned)

All these instructions belong to the B-type ones (figure 2). They have an immediate field split along the word, which indicates an effective immediate divided by two. Indeed, with a RISC-V standard architecture it is possible to address this way an halfword at most, but never the single byte. The effective immediate is calculated with a bit reorganization, a sign extension and a left shift of one position, to reach the final 32-bit width.

The instruction contains also the addresses of two registers, whose content will be compared by the ALU to decide whether to take the branch or not. To distinguish which type of comparison is needed, it is necessary to know the instruction field funct3.

**Jump** instructions can be of two types, each bringing to a different hardware path for the data:

1. JAL
2. JALR

**JAL** is a J-type instruction, whereas **JALR** is an I-type one. This difference is reflected on the hardware implementation, more on this later. A jump instruction is unconditional, but still need for an address computation. This operation is different for the two instructions: for JAL it is sufficient to use the same hardware used for branch address computation, whereas JALR requires the non shifted immediate to be added to the content of a register (the next address is not derived by the current one).

### 2.3.2 Instruction execution

Since no **BPU** (**B**ran**P**rediction **U**nit) is present in the design, a "branch not taken" assumption is always made when the content of the PC is updated and the decoded instruction is a branch. The simplest way to manage a branch is to delay the decision until the execution stage, waiting for the ALU to do the comparison. The effective decision is then taken in the DMEM stage, not to exacerbate a path which can be critical by itself. Also the calculation of the next address, which involves the immediate and the program counter, is performed in the execution stage.

A possible improvement could be to anticipate the comparison and the next address calculation in the decoding stage, but to keep the design simple the first solution was chosen, as this would imply additional hardware. This is compliant with the calculation of the address for a JAL instruction. It is worth to mention that the absence of a condition to be verified is enough to simplify the anticipation of the address calculation and bring it in the decode stage. However this solution would increase the number of resources if the other branch/jump instructions are still executed in an another stage.

A JALR instruction behaves in a slightly different way: the address calculation is performed by the ALU, because the immediate is added to the content of a register.

A branch instruction has no side effects once it has been executed. On the contrary, a jump instruction leaves inside the pipeline the next instruction address to be saved in a destination register. This is not a issue though, because it is possible to see that even without forwarding units no data hazards can arise. If the pipeline was longer, maybe the forwarding unit would be the only thing to have the day saved (the design has it, though).

### 2.3.3 Effective calculation

The address calculation in case of branches/jumps is performed in the execution stage and it depends on the type of instruction:

- Branch/JAL: it is based on the "current" PC value (e.g. current for the instruction in that stage). The immediate is sign extended, one position left shifted and added to the PC value (percolated through the pipeline until there) by means of another adder. In the meantime, if the instruction is a JAL, the address of the next instruction goes on through the stages.
- JALR: it involves a sum between an immediate and the content of a register. The ALU performs this operation without shifting the immediate. When the result has to be used, the LSB is substituted with a zero. Even in this case, the address of the next instruction follows its path towards the write-back stage.



### 2.3.4 Next address selection CU

To control the multiplexers for the next address selection, there's the need for knowing:

1. Whether the instruction in the DMEM stage is a branch or a jump.
2. Which is between the two.
3. The result of the comparison.
4. If the instruction is a JALR.

The main CU generates two signals **branch** and **jump** which percolate along the pipeline, to allow the "Next address selection CU" to solve the first two points. The result of a comparison is simply the LSB of the ALU result. The main CU thus has to generate another signal **jalr** to indicate a JALR instruction.

The **jump** control signal is used also in the write-back stage, to select the right input for the register file. If a jump is performed, the data to be written in the destination register is the "next" address after the jump instruction.

In any case, the IMEM pipe register, together with IF/ID, ID/EX and EX/DMEM ones, have to be flushed. This brings to a performance loss of 4 instructions for each taken branch or executed jump.

For details about the **NEXT\_ADDR\_SEL\_CU**, refer to figure 9 and 10.

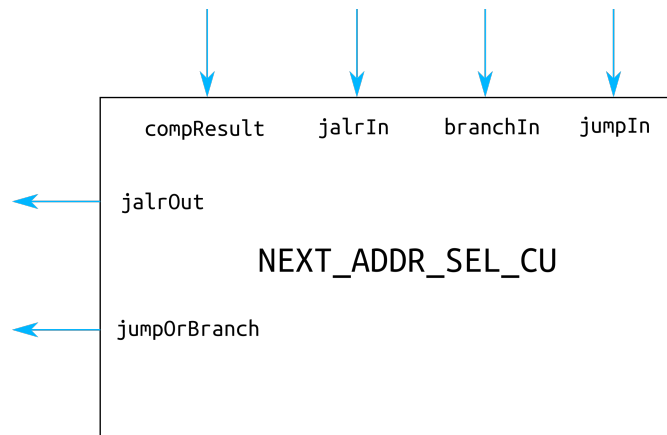


Figure 9: Next address selection CU, for jumps and branch management

*NEXT\_ADDR\_SEL\_CU internal logic*

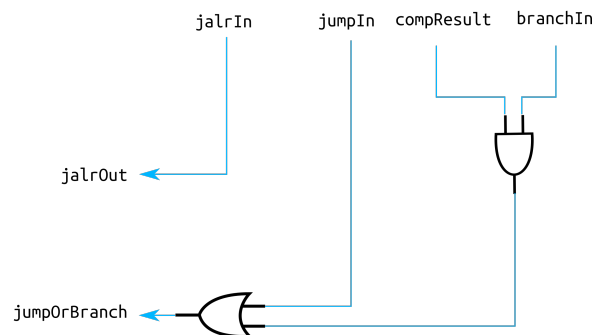


Figure 10: Next address selection CU internal logic

### 2.3.5 Next address generation

The next address is chosen by means of two multiplexers:

- BRJAL\_JALR\_MUX takes in input the result of the ALU with the LSB masked and the output of the additional adder of the execution stage. These two input come from the EX/DMEM pipe register.
- NEXT\_PC\_MUX takes in input the output of BRJAL\_JALR\_MUX and the current PC + 4

### 3 Control

#### 3.1 Forwarding Unit (FWU)

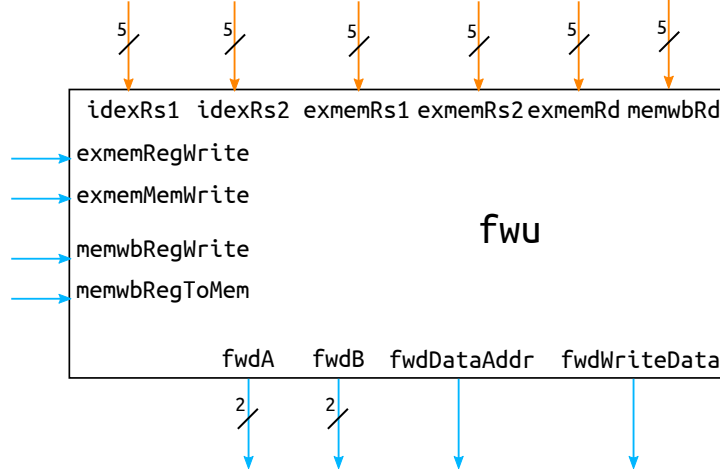


Figure 11: Forwarding Unit

Forwarding allows to avoid stalling the pipeline when a data hazard occurs between two subsequent instructions, if the needed data is already available in a following pipe stage. In this five stage pipeline results are written to the destination register during the write back stage, three clock cycles after the operand read in the decode stage. This means that, if an instruction modifies a certain register, only instructions starting from the third after the original would read the correct new data, or equivalently that up to two bubble should be inserted in case of a data hazard.

Forwarding simply bypasses data to the beginning of the execution stage (i.e. at the ALU inputs) if the required results are already present at the ALU output or in the following memory access stage.

To do so, the logic of the FWU (figure 11) performs some checks:

- Check that the earlier in the pipe actually modifies some register (`regWrite` is asserted) and that the address does not point to register `x0`.
- Compare the destination register in the EX/MEM stage with both source register in the ID/EX stage and, if there is a match, drives the selection signal of the corresponding ALU input multiplexer to select the previous ALU output (`fwdA/fwdB = 10`).
- Otherwise, compare the destination register in the MEM/WB stage with both source register in the ID/EX stage and, if there is a match, drives the selection signal of the corresponding ALU input multiplexer to select the result currently in the memory access stage (`fwdA/fwdB = 01`).

Note that, according to the list above, forwarding gives precedence to data present in the EX/MEM stage over the MEM/WB stage if the same register is present in both, as the former contains the latest result.

##### 3.1.1 Load/store forwarding

The designed forwarding unit handles also the another special case of data hazard that occurs when a load is followed immediately by a store to the same memory location, such as in memory to memory copies.

In this case the FWU checks that the two involved instructions are actually a load (`memToReg` asserted in the MEM/WB stage) and a store (`memWrite` asserted in the EX/MEM stage) and that the destination and source registers are the same, and if that is the case drives the control of the multiplexer selecting the memory data input to choose the memory output.

Figure 12 shows the FWU with all inputs on which decisions are taken and the three output signals controlling the related multiplexers in each pipeline stage of the core.

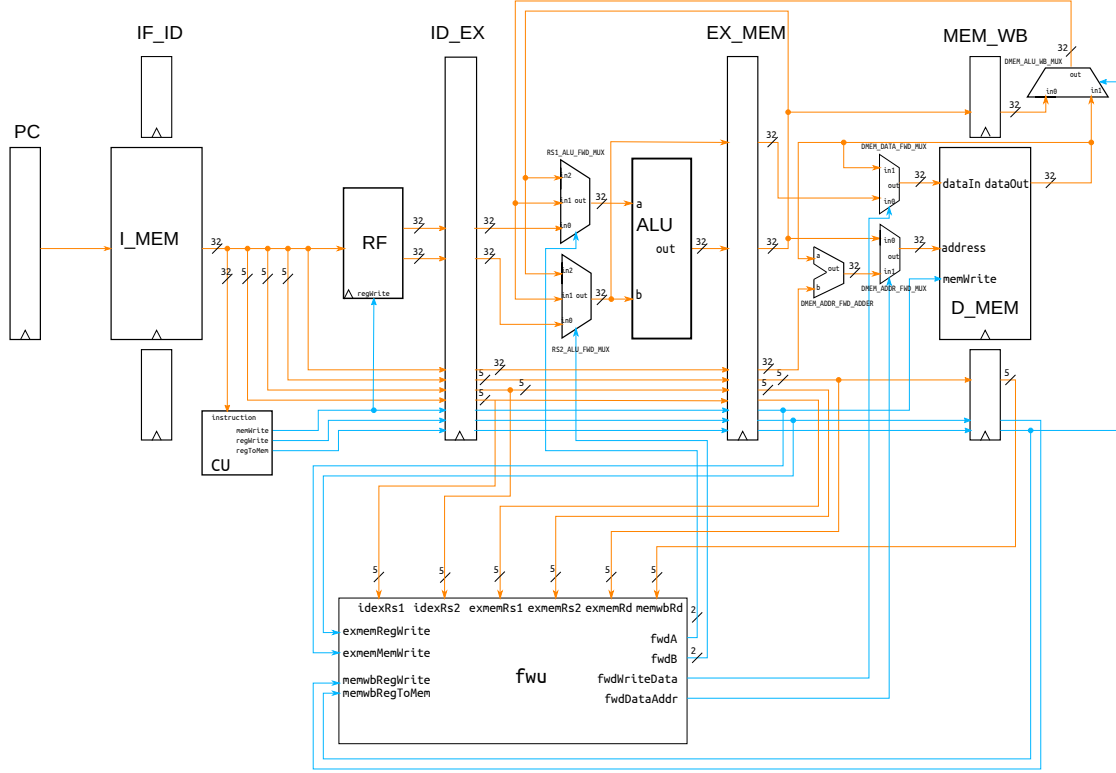


Figure 12: Forwarding Unit connection to the datapath of the core

### 3.2 Hazard Detection Unit (HDU)

When data cannot be forwarded, then the pipeline must be inevitably stalled by preventing the fetch of a new instruction and inserting a bubble. Specifically, this happens when a data hazard occurs between a load (`memRead` asserted in the decode stage) and another using instruction (unless it is a store, for which forwarding accounts).

Moreover, when a branch is taken or an unconditional jump occurs, a similar action of flushing the entire pipeline to get rid of invalid instructions already in execution must be taken.

Both these occurrences are handled by the Hazard Detection Unit (figure 13), that according to the aforementioned checks, outputs three signals:

- **stall\_n**: active low, is connected to the enable of the Program Counter and the IF/ID pipe register to prevent them from changing in the event of a stall.
- **flushIdEx**: to drive the multiplexer inserting the NOP in the ID/EX register, that will propagate to the rest of the pipeline, in case of a stall or a jump.
- **flushIfIdExMem**: to drive the multiplexer inserting the NOP in the IF/ID and EX/MEM registers in case of jump.

A summary of the possible cases when this can occur is reported in table 1:

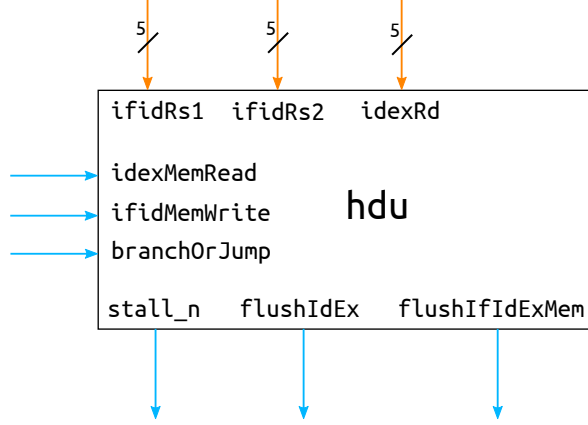


Figure 13: Hazard Detection Unit

	stall_N	flush_IdEx	flush_IfId_ExDmem
<b>No Hazard</b>	0	0	0
<b>Control Hazard</b>	0	1	1
<b>Data Hazard</b>	1	1	0

Table 1: HDU output

### 3.2.1 Inserting a NOP

The NOP instruction is not present in the RISC-V ISA. It is possible to emulate it though, using an `ADDI x0 x0 0`. This instruction does nothing, because the register `x0` is hardwired to value 0. The instruction NOP belongs to the set of pseudo-assembly instructions: they are translated in RISC-V language on the fly by the assembler, and they exist for programmers ease only.

For an effective NOP insertion in the IF/ID stage there is the need for a sequential control of the multiplexer which drive the source of the RF. There is no way of doing it before the pipe register, unless a NOP instruction is already present somewhere in memory.

In figure 14 a high level datapath for hazard management is depicted. Moreover, a timing diagram to show how instructions are flushed is shown in figure 15. The three instructions which follow a jump or a taken branch are discarded.

## 3.3 Control Unit (CU)

The Control Unit is shown in figure 16. It is a combinational component, because all the synchronization is done in the pipeline registers. It basically reads the opcode and other eventual flags (`funct3`, `funct7`) to determine the format of the instruction used in the immediate generator, as well as other flags.


These flags are about memory commands (read, write, how much to read/write), register-file commands (write, address is generated in the remaining datapath), MUX commands (to decide the inputs to use for the ALU) and branch/jump commands.

There are two commands which are a bit less standardized, to tell the memory the dimension to access (byte, halfword, word) and to tell apart the different jump conditions like branch, jal, jalr.

It is implemented in a behavioral way, to avoid possible risks, and all the parameters are defined as constants, to be easily updated if needed.
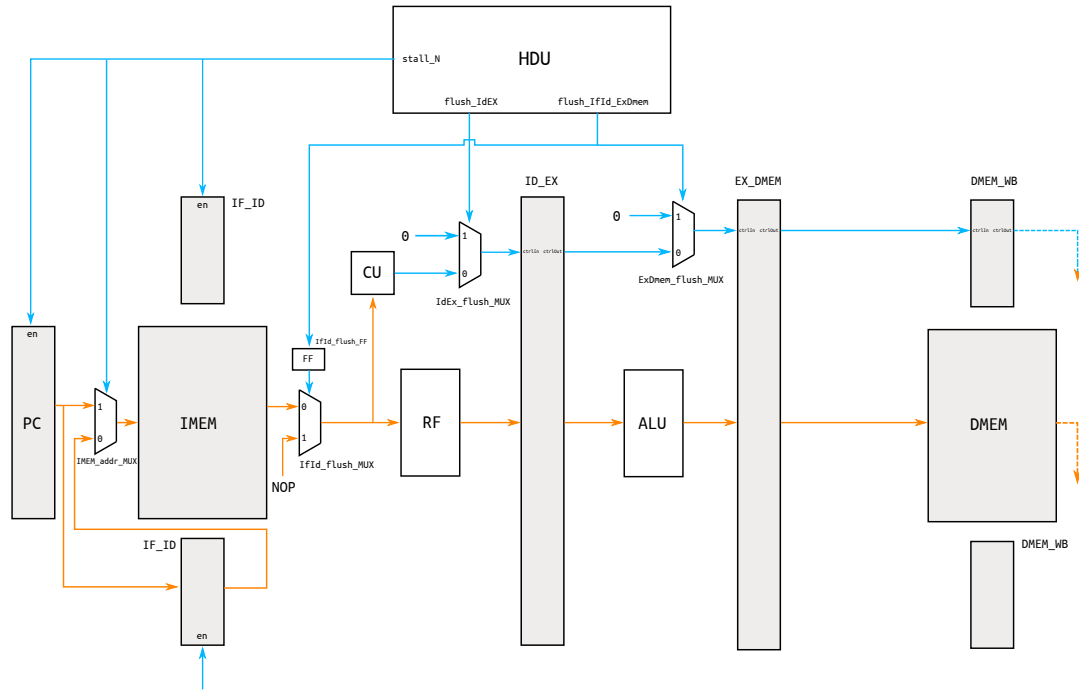
## 3.4 Immediate Generator (ImmGen)

The Immediate Generator (show in figure 17) is needed to gather the correct bits from the different instruction formats. The type of instruction is signalled by the Control Unit, and the output is the reconstructed immediate in the same cycle, since it is a combinational component.



NOP = ADDI x0, x0, 0, 0 = 000000000000 00000 000 00000 0010011

Figure 14: Hazard management HW

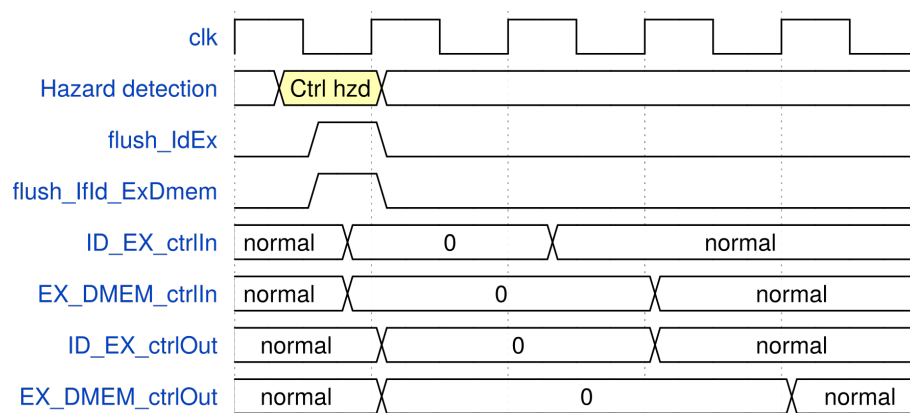


Figure 15: Hazard management timing

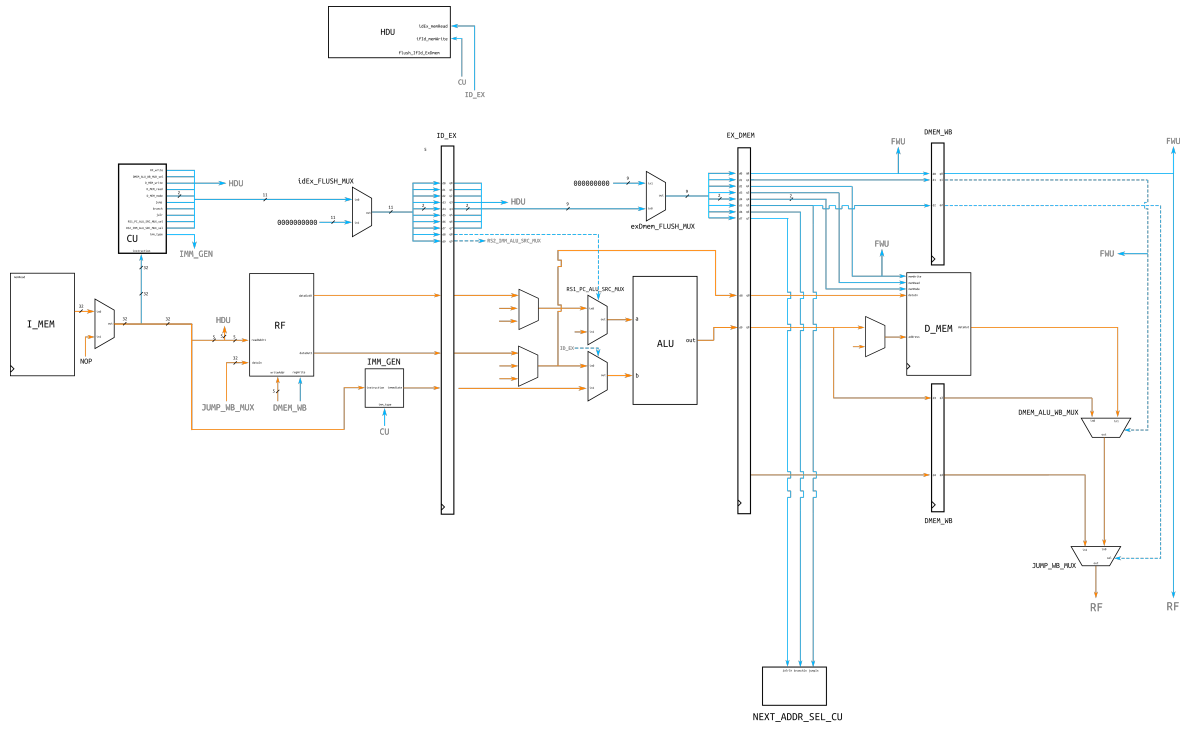


Figure 16: Control Unit and the units connected to it

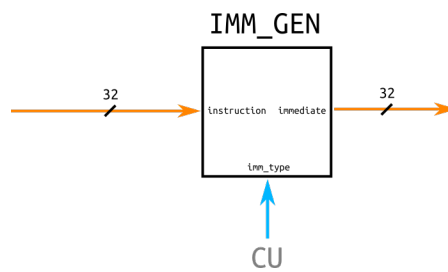


Figure 17: Immediate Generator

The main architecture is depicted in figure 18. One multiplexer was added in the execution stage to add the support for the AUIPC operation.



## 5.1 Memory

This model is only intended for simulation purposes and does not map a real memory chip on its own, but emulates the function of a more complex memory controller able to select individual bytes among a 32-bit word both in read and in write operations.

- 00: byte
- 01: halfword (16 bits)
- 10: word (32 bits)

Read and write operations are handled by the couple of control signals `memRead` and `memWrite`, of which only one should be asserted at each clock cycle to perform the desired action. Both signals active represent an forbidden condition and should be avoided by the whatever is in charge of controlling the memory.

## 5.2 Testing procedure

15

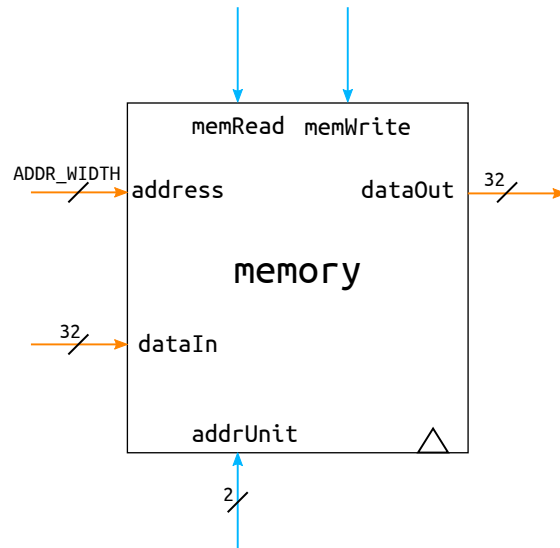


Figure 19: Memory

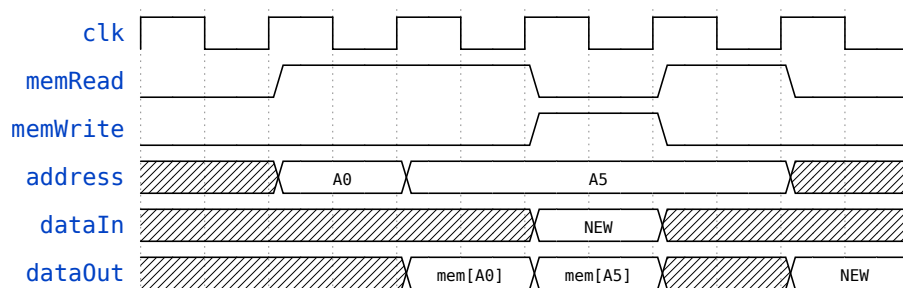


Figure 20: Memory timing diagram



1. the correct behavior of each instruction in a flow without hazards
2. the correct management of all the hazards

To achieve this in an easier way, an assembler was developed to support a translation from the RISC-V assembly to the machine code. A detailed discussion about this tool is provided in section 5.3. Initially a search on the net was done to find a toolchain to convert high level languages like C in RV32I instructions, but a lot of issues arose and other strategies were chosen. The developing of an assembler is not critical, because of its static nature: it works like a decoder and it does not need to be “clever” like a compiler. Testing needs weren’t critical and a string check processing was enough.

### 5.2.1 Testbench

The testbench was written in SystemVerilog coherently with all the previous work. The entity instantiates the **DUV** (**D**evice **U**nder **V**erification) together with the two memories. It also handles the clock and reset generation. It is worth to note that the addressable space of the memory was reduced because a complete 32-bit one was not feasible due to space problems: only a subset of the PC bits was bound to the address line of the storage devices.

The entire system is reset at the beginning of the simulation, and a parametric clock is fed to all the sequential elements. An `initial` statement inside the memory modules ensures the correct loading of the instructions/data inside them. To perform this task, the function `$readmemh` is used: it allows to read an ASCII text file in which are present hexadecimal data written in rows. Each row is assigned to a memory location.

With the aid of the ModelSim GUI, each signal was visually followed to check if the timing of the processor was respected.

### 5.2.2 Single instructions test

First of all each instruction was individually tested to assure the correct behavior of the whole pipeline mechanism.

**Register loads** To test each register of the register file, as well as to make sure that register `x0` does not change, a series of consecutive `lui` instructions was used, trying with both positive and negative values. The `auipc` instruction was tested as well at this point.

```
lui x0, 37
lui x1, 133
lui x2, 65
lui x3, -1
lui x4, 0
...
auipc x2, 6466
```

As an example, figure 21 shows the completion of the register file loading test.

**Immediate ALU instructions** Next, we tried all ALU operations involving immediate operands.

```
addi x4, x3, -56
andi x6, x5, 255
ori x8, x7, 255
xori x10, x9, 255
slli x12, x11, 3
srli x14, x13, 4
srai x16, x15, 8
slti x18, x17, 0
sltiu x20, x19, 5
```

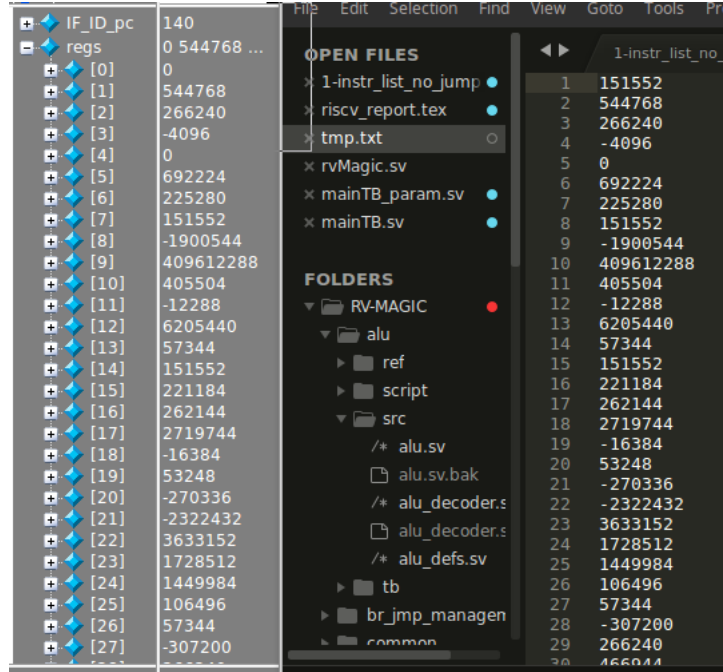


Figure 21: RF loading verification

**Register ALU instructions** Then, the same instructions were tried with both operands being read from the register file.

```
add x23, x21, x22
sub x26, x24, x25
and x29, x27, x28
or x1, x30, x31
xor x4, x2, x3
sll x7, x5, x6
srl x10, x8, x9
srai x13, x11, 12
slt x16, x14, x15
sltu x19, x17, x18
```

**Load and stores** Finally all load and stores were tested, on all the different data widths.

```
lb x21, 3(x20)
lh x23, 8(x22)
lbu x25, 34(x24)
lhu x27, 45(x26)
lw x29, 9(x28)

sb x31, 3(x30)
sh x2, 23(x1)
sw x4, 89(x3)
```

### 5.2.3 Branches and control hazard test

The next step was the test of all kinds of branch instructions, both taken and not taken, to verify at the same time the correct behavior of the HDU in case of taken branch and subsequent stall.

**Unconditional jumps** First of all, the two unconditional jump instructions were tested, namely `jal` and `jalr`. The initial `addi` of the second case was inserted only to have a known value in register `x3`.

```

jal x2, 2

addi x3, x0, 5
nop
nop
jalr x4, x3, 3

```

In this case, the important things to notice are the correct evolution of the program counter after the jump (along with the right generation of the address and LSB masking) and the correct generation of the CU signals `jumpOrBranch` and `jalr`, as well as `stall_n` from the HDU, to disable the PC and the IF/ID pipe register.

**Branches** A similar procedure was used to test branches.

```

addi x1, x0, 9
addi x2, x0, 9
nop
nop
beq x1, x2, 16

```

#### 5.2.4 Data hazards and forwarding

The last set of instructions was aimed at testing the correct behavior of the HDU and FWU under all conditions.

The first case is the forwarding of the previous ALU result:

```

addi x1, x0, 56
and x3, x1, x2

```

Next, forwarding can also occur from the ALU result of two cycles earlier:

```

addi x13, x1, 253
sub x7, x5, x6
xor x3, x13, x2

```

Finally, forwarding between load and store was tested:

```

addi x1, x0, 45
nop
nop
lw x2, 16(x1)
sw x2, 32(x1)

```

The hazard detection was tested with a load followed by another using instruction:

```

lw t0, 0(x0)
addi x1, t0, 1

```

In all the previous cases, the focus was on the interface signals of the HDU and FWU, as well as the correct stalling and flushing of the pipeline.

#### 5.2.5 Complete program test


After having tested all single instructions and hazard scenario individually, a complete assembly program was tested, in order to verify the correctness of the design in a real application. The program in question (listed below) is the translation to RISC-V assembly of the test program provided for the laboratory experience on the MIPS processor, which computes the minimum absolute value among the elements of a vector.


```

#_start:
li x1, 7          # load x1 with 7 (number of elements)    0
li x2, 16         # put in x2 the address of v (16)        4
li x3, 8          # put in x3 the address of m (8)         8

```

lw x4, 0(x3)	# init x4 with max value (high)	12
#loop:		
beq x1, x0, 48	# check all elements have been tested	16
lw x5, 0(x2)	# load new element in x5	20
srai x6, x5, 31	# apply shift to get sign mask in x6	24
xor x7, x5, x6	# x7 = sign(x5)^x5 (invert x5 if negative)	28
andi x6, x6, 1	# x6 &= 1 (carry in)	32
add x7, x7, x6	# x7 += x6 (add the carry in)	36
addi x2, x2, 4	# point to next element	40
addi x1, x1, -1	# decrease x1 by 1	44
slt x8, x7, x4	# x8 = (x7 < x4) ? 1 : 0	48
beq x8, x0, -36	# next element	52
add x4, x7, x0	# update min	56
jal x0, -44	# next element	60
#done:		
sw x4, 0(x3)	# store the result	64

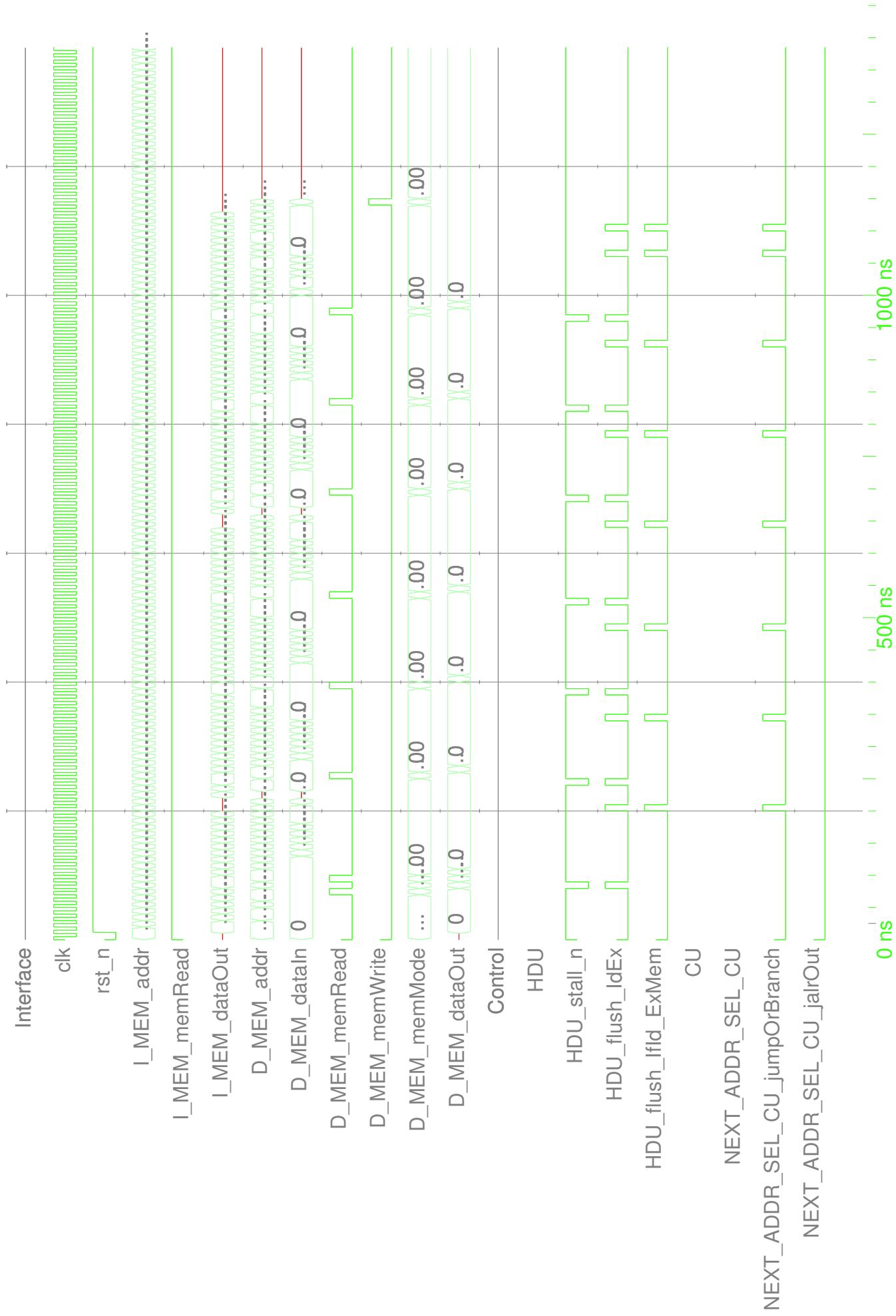

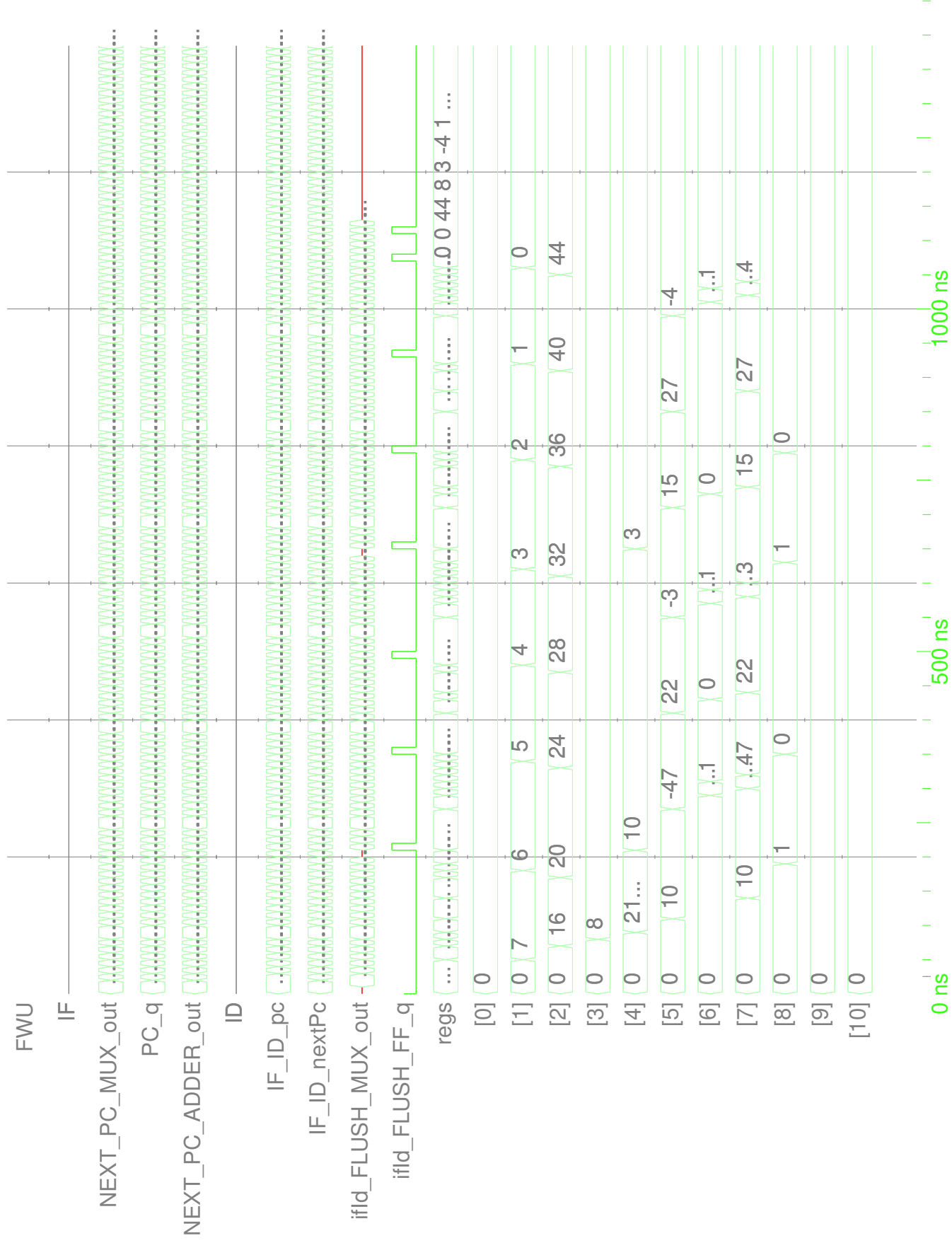

### 5.3 Assembler